

Problem 1

A car battery with a 12 V emf and an internal resistance of $0.040\ \Omega$ is being charged with a current of 50 A. What are (a) the potential difference V across the terminals, (b) the rate P_r of energy dissipation inside the battery, and (c) the rate P_{emf} of energy conversion to chemical form? When the battery is used to supply 50 A to the starter motor, what are (d) V and (e) P_r ? (05小題)

When the battery is being charged:

(a) _____ V

01: ANS:=14

(a) The potential difference is $V = \mathcal{E} + ir = 12\ \text{V} + (50\ \text{A})(0.040\ \Omega) = 14\ \text{V}$.

(b) _____ W

02: ANS:=1.0E2

(b) $P = i^2 r = (50\ \text{A})^2(0.040\ \Omega) = 1.0 \times 10^2\ \text{W}$.

(c) _____ W

03: ANS:=6.0E2

(c) $P' = iV = (50\ \text{A})(12\ \text{V}) = 6.0 \times 10^2\ \text{W}$.

When the battery is used:

(d) _____ V

(d) In this case $V = \mathcal{E} - ir = 12\ \text{V} - (50\ \text{A})(0.040\ \Omega) = 10\ \text{V}$.

04: ANS:=10


(e) $P_r = i^2 r = (50\ \text{A})^2(0.040\ \Omega) = 1.0 \times 10^2\ \text{W}$.

(e) _____ W

05: ANS:=1.0E2

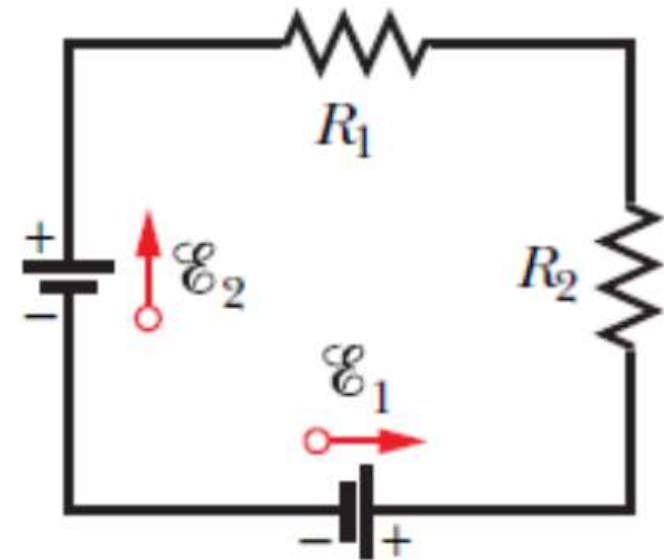Problem 2

In the figure, the ideal batteries have emfs $\epsilon_1 = 12 \text{ V}$ and $\epsilon_2 = 6.0 \text{ V}$ and the resistors have resistances $R_1 = 4.0 \text{ }\Omega$ and $R_2 = 8.0 \text{ }\Omega$. What are (a) the current, the dissipation rate in (b) resistor 1 and (c) resistor 2, and the energy transfer rate in (d) battery 1 and (e) battery 2? Is energy being supplied or absorbed by? (05小題)



(a) _____ A

06: ANS:=0.5

(b) $P_{R_1} =$ _____ W

07: ANS:=1.0

(c) $P_{R_2} =$ _____ W

08: ANS:=2.0

(d) $P_{\epsilon_1} =$ _____ W

09: ANS:=6.0

(e) $P_{\epsilon_2} =$ _____ W

10: ANS:=3.0

$$(a) \epsilon_1 - iR_2 - iR_1 - \epsilon_2 = 0. \quad i = \frac{\epsilon_1 - \epsilon_2}{R_1 + R_2} = \frac{12 \text{ V} - 6.0 \text{ V}}{4.0 \text{ }\Omega + 8.0 \text{ }\Omega} = 0.50 \text{ A.}$$

$$(b) \text{ For } R_1, P_1 = i^2 R_1 = (0.50 \text{ A})^2 (4.0 \text{ }\Omega) = 1.0 \text{ W,}$$


$$(c) \text{ and for } R_2, P_2 = i^2 R_2 = (0.50 \text{ A})^2 (8.0 \text{ }\Omega) = 2.0 \text{ W.}$$

$$(d) \text{ For } \epsilon_1, P_1 = i\epsilon_1 = (0.50 \text{ A})(12 \text{ V}) = 6.0 \text{ W}$$

$$(e) \text{ and for } \epsilon_2, P_2 = i\epsilon_2 = (0.50 \text{ A})(6.0 \text{ V}) = 3.0 \text{ W.}$$

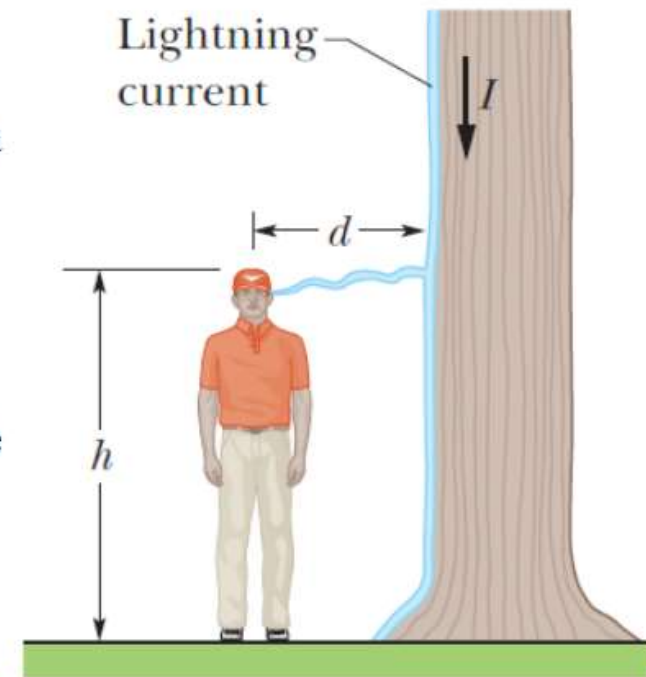Problem 3

Side flash. The figure indicates one reason no one should stand under a tree during a lightning storm. If lightning comes down the side of the tree, a portion can jump over to the person, especially if the current on the tree reaches a dry region on the bark and thereafter must travel through air to reach the ground. In the figure, part of the lightning jumps through distance d in air and then travels through the person (who has negligible resistance relative to that of air). The rest of the current travels through air alongside the tree, for a distance h . If $d/h = 0.400$ and the total current is $I = 5000 \text{ A}$, what is the current through the person? (01小題)



_____ A

11: ANS:=3571

across the two paths are the same, $V_1 = V_2$ $i_1 R_1 = i_2 R_2$, $i = i_1 + i_2 = 5000 \text{ A}$.


$$R = \rho L / A \quad i_1 d = i_2 h \Rightarrow i_2 = i_1 (d / h).$$

With $d/h = 0.400$, we get $i_1 = 3571 \text{ A}$ and $i_2 = 1429 \text{ A}$

the current through the person is $i_1 = 3571 \text{ A}$

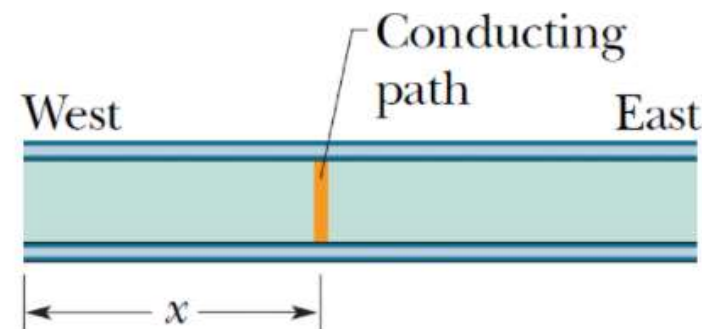Problem 4

A 10-km-long under-ground cable extends east to west and consists of two parallel wires, each of which has resistance $13 \Omega/\text{km}$. An electrical short develops at distance x from the west end when a conducting path of resistance R connects the wires (the figure). The resistance of the wires and the short is then 100Ω when measured from the east end and 200Ω when measured from the west end. What are (a) x and (b) R ? (02小題)



(a) $x =$ _____ km

12: ANS: = 6.9

(b) $R =$ _____ Ω

13: ANS: = 20

(a) We denote $L = 10 \text{ km}$ and $\alpha = 13 \Omega/\text{km}$. Measured from the east end we have

$$R_1 = 100 \Omega = 2\alpha(L - x) + R,$$

and measured from the west end $R_2 = 200 \Omega = 2\alpha x + R$. Thus,


$$x = \frac{R_2 - R_1}{4\alpha} + \frac{L}{2} = \frac{200 \Omega - 100 \Omega}{4(13 \Omega/\text{km})} + \frac{10 \text{ km}}{2} = 6.9 \text{ km}.$$

(b) Also, we obtain

$$R = \frac{R_1 + R_2}{2} - \alpha L = \frac{100 \Omega + 200 \Omega}{2} - (13 \Omega/\text{km})(10 \text{ km}) = 20 \Omega.$$

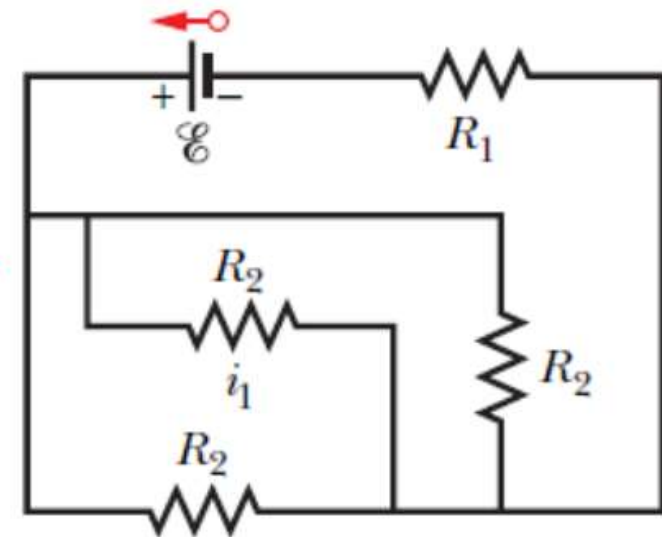Problem 5

In the figure, $R_1 = 6.00 \Omega$, $R_2 = 18.0 \Omega$, and the ideal battery has emf $\mathcal{E} = 12.0 \text{ V}$. What are the (a) size and (b) How much energy is dissipated by all four resistors in 1.00 min? (02小題)



(a) _____ A

14: ANS:=0.333

(b) _____ J

15: ANS:=720

(a) The parallel set of three identical $R_2 = 18 \Omega$ resistors reduce to $R = 6.0 \Omega$, which is now in series with the $R_1 = 6.0 \Omega$ resistor at the top right, so that the total resistive load across the battery is $R' = R_1 + R = 12 \Omega$. Thus, the current through R' is $(12\text{V})/R' = 1.0 \text{ A}$, which is the current through R . By symmetry, we see one-third of that passes through any one of those 18Ω resistors; therefore, $i_1 = 0.333 \text{ A}$.

(b) We use Eq. 26-27: $P = i^2 R' = (1.0 \text{ A})^2 (12 \Omega) = 12 \text{ W}$. Thus, in 60 s, the energy dissipated is $(12 \text{ J/s})(60 \text{ s}) = 720 \text{ J}$.

Problem 6

The current in a single-loop circuit with one resistance R is 5.0 A. When an additional resistance of 2.0Ω is inserted in series with R , the current drops to 4.0 A. What is R ? (01小題)

_____ Ω

16: ANS:=8.0

Let the emf be V . Then $V = iR = i'(R + R')$, where $i = 5.0 \text{ A}$, $i' = 4.0 \text{ A}$ and $R' = 2.0 \Omega$. We solve for R :

$$R = \frac{i'R'}{i - i'} = \frac{(4.0 \text{ A})(2.0 \Omega)}{5.0 \text{ A} - 4.0 \text{ A}} = 8.0 \Omega.$$

Problem 7

In the figure, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$, and the ideal batteries have emfs $\epsilon_1 = 6.0 \text{ V}$, $\epsilon_2 = 5.0 \text{ V}$, and $\epsilon_3 = 4.0 \text{ V}$. Find (a) the current in resistor 1, (b) the current in resistor 2 (absolute value), and (c) the potential difference between points a and b . (03小題)

(a) _____ A

17: ANS:=0.050

(b) _____ A

18: ANS:=0.06

(c) _____ V

19: ANS:=9.0


Let i_1 take it to be positive if it is to the right.
 i_2 take it to be positive if it is upward.

$$\epsilon_2 - i_1 R_1 = 0. \quad i_1 = \frac{\epsilon_2}{R_1} = \frac{5.0 \text{ V}}{100 \Omega} = 0.050 \text{ A}.$$

$$\epsilon_1 - \epsilon_2 - \epsilon_3 - i_2 R_2 = 0.$$

$$i_2 = \frac{\epsilon_1 - \epsilon_2 - \epsilon_3}{R_2} = \frac{6.0 \text{ V} - 5.0 \text{ V} - 4.0 \text{ V}}{50 \Omega} = -0.060 \text{ A}, \quad |i_2| = 0.060 \text{ A}.$$


$$V_a = V_b + \epsilon_3 + \epsilon_2, \quad V_a - V_b = \epsilon_3 + \epsilon_2 = 4.0 \text{ V} + 5.0 \text{ V} = 9.0 \text{ V}.$$

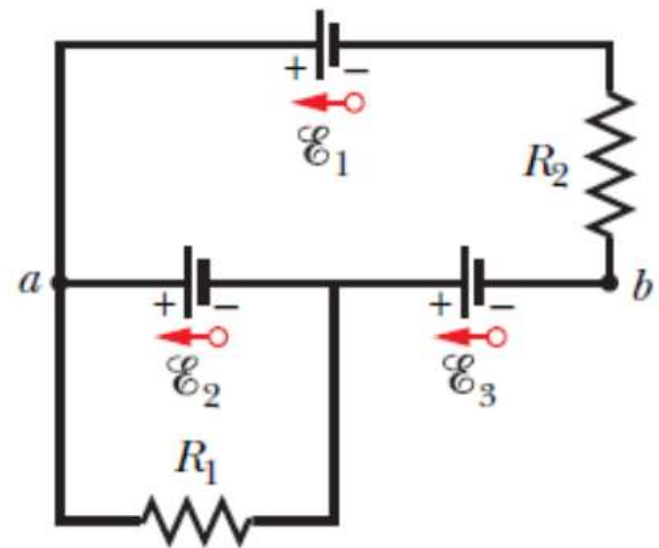

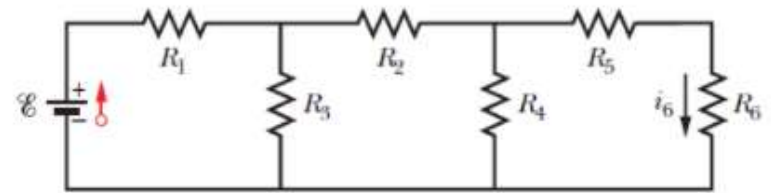Problem 8

In the figure, the current in resistance 6 is $i_6 = 1.40$ A and the resistances are $R_1 = R_2 = R_3 = 2.00$ Ω , $R_4 = 16.0$ Ω , $R_5 = 8.00$ Ω , and $R_6 = 4.00$ Ω .

What is the emf of the ideal battery? (01小題)



_____ V

V_4 is equal to the sum of the voltages across R_5 and R_6 :

20: ANS:=48.3

$$V_4 = i_6(R_5 + R_6) = (1.40 \text{ A})(8.00 \Omega + 4.00 \Omega) = 16.8 \text{ V.}$$

$$i_4 = V_4/R_4 = 16.8 \text{ V}/(16.0 \Omega) = 1.05 \text{ A.}$$

$$i_2 = i_4 + i_6 = 1.05 \text{ A} + 1.40 \text{ A} = 2.45 \text{ A.}$$

$$V_2 = (2.00 \Omega)(2.45 \text{ A}) = 4.90 \text{ V.}$$

The loop rule tells us the voltage across R_3 is

$$V_3 = V_2 + V_4 = 21.7 \text{ V}$$

$$i_3 = V_3/(2.00 \Omega) = 10.85 \text{ A}$$


$$i_1 = i_2 + i_3 = 2.45 \text{ A} + 10.85 \text{ A} = 13.3 \text{ A.}$$

$$V_1 = (13.3 \text{ A})(2.00 \Omega) = 26.6 \text{ V.}$$

$$\mathcal{E} = V_1 + V_3 = 26.6 \text{ V} + 21.7 \text{ V} = 48.3 \text{ V.}$$

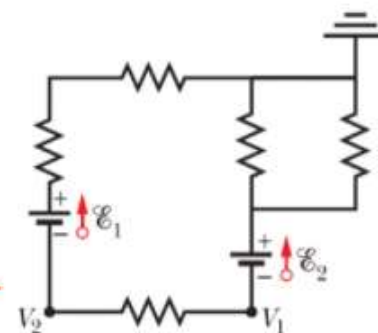Problem 9

In the figure, the ideal batteries have emfs $\mathcal{E}_1 = 5.0 \text{ V}$ and $\mathcal{E}_2 = 12.0 \text{ V}$, the resistances are each 2.0Ω , and the potential is defined to be zero at the grounded point of the circuit. What are potentials (a) V_1 and (b) V_2 at the indicated points? (02小題)




(a) $V_1 = \underline{\hspace{2cm}} \text{ V}$

21: ANS:=-11

(b) $V_2 = \underline{\hspace{2cm}} \text{ V}$

22: ANS:=-9

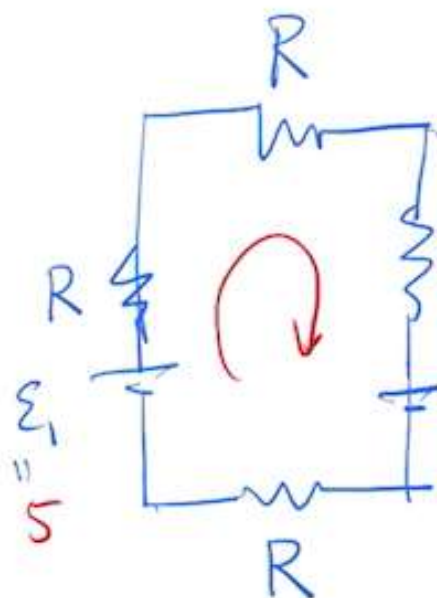

$$R' = \frac{R}{2} = 1$$

$$\mathcal{E}_2 = 12$$

$$R = 2$$




$$V_1 + 12 + (-1)(1)$$

$$V_1 = -11$$

$$\mathcal{E}_1 - (R' + 3R)I - \mathcal{E}_2 = 0$$

$$5 - \frac{7}{2}IR - 12 = 0$$

$$I = -1$$

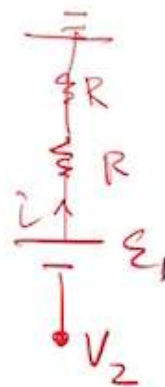


$$V_2 + 5 - (-1)(4) = 0$$

$$V_2 = -9$$

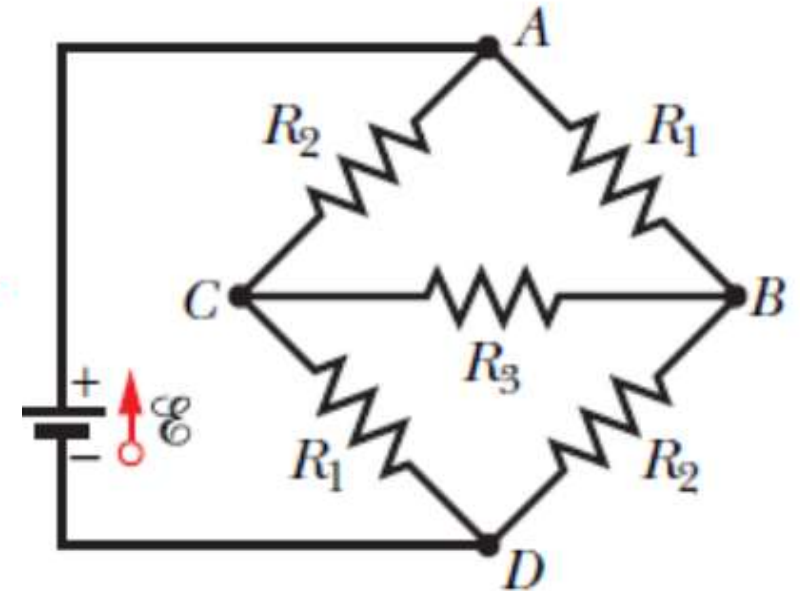Problem 10

In the figure, $\epsilon = 12.0 \text{ V}$, $R_1 = 2000 \Omega$, $R_2 = 3000 \Omega$, and $R_3 = 4000 \Omega$. What are the potential differences (a) $V_A - V_B$, (b) $V_B - V_C$, (c) $V_C - V_D$, and (d) $V_A - V_C$? (04/小題)



(a) $V_A - V_B = \underline{\hspace{2cm}} \text{ V}$

$$i_3 = i_1 - i_2.$$

23: ANS:=5.25

$$\epsilon - i_2 R_2 - i_1 R_1 = 0$$

(b) $V_B - V_C = \underline{\hspace{2cm}} \text{ V}$

$$\epsilon - 2i_1 R_1 - (i_1 - i_2) R_3 = 0$$

24: ANS:=1.50

$$i_1 = 0.002625 \text{ A}, \quad i_2 = 0.00225 \text{ A}$$

(c) $V_C - V_D = \underline{\hspace{2cm}} \text{ V}$

$$i_3 = i_1 - i_2 = 0.000375 \text{ A}.$$

25: ANS:=5.25

$$V_A - V_B = i_1 R_1 = 5.25 \text{ V}.$$

(d) $V_A - V_C = \underline{\hspace{2cm}} \text{ V}$

(b) It follows also that $V_B - V_C = i_3 R_3 = 1.50 \text{ V}$.

26: ANS:=6.75

(c) We find $V_C - V_D = i_1 R_1 = 5.25 \text{ V}$.

(d) Finally, $V_A - V_C = i_2 R_2 = 6.75 \text{ V}$.

Problem 11

What multiple of the time constant τ gives the time taken by an initially uncharged capacitor in an RC series circuit to be charged to 99.0% of its final charge? (01小題)

_____ τ

27: ANS:=4.61

$$q = C\varepsilon(1 - e^{-t/\tau}), \quad \tau = RC$$

C is the capacitance, ε is applied emf,

$q_{\text{eq}} = C\varepsilon$. The equilibrium charge

$$q = 0.99q_{\text{eq}} = 0.99C\varepsilon,$$


$$0.99 = 1 - e^{-t/\tau}.$$

$$e^{-t/\tau} = 0.01.$$

$$t/\tau = -\ln 0.01 = 4.61 \text{ or } t = 4.61 \tau$$

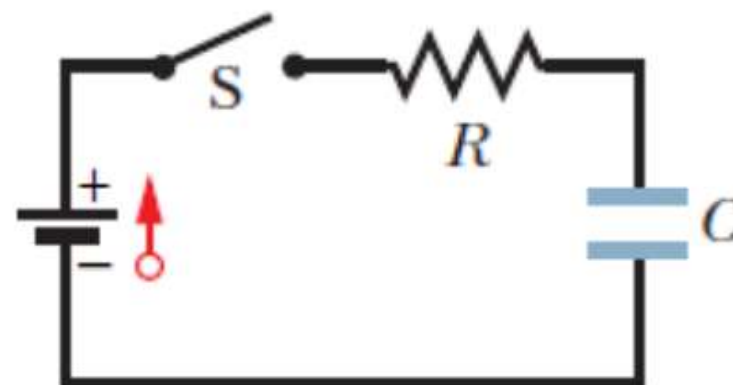Problem 12

Switch S in the figure is closed at time $t = 0$, to begin charging an initially uncharged capacitor of capacitance $C = 15.0 \mu\text{F}$ through a resistor of resistance $R = 20.0 \Omega$. At what time is the potential across the capacitor equal to that across the resistor? (01小題)



_____ ms

28: ANS:=0.208


the resistor voltage be equal to the capacitor voltage becomes $iR = V_{\text{cap}}$, or

$$Ve^{-t/RC} = V(1 - e^{-t/RC})$$

This leads to $t = RC \ln 2$, or $t = 0.208 \text{ ms}$.

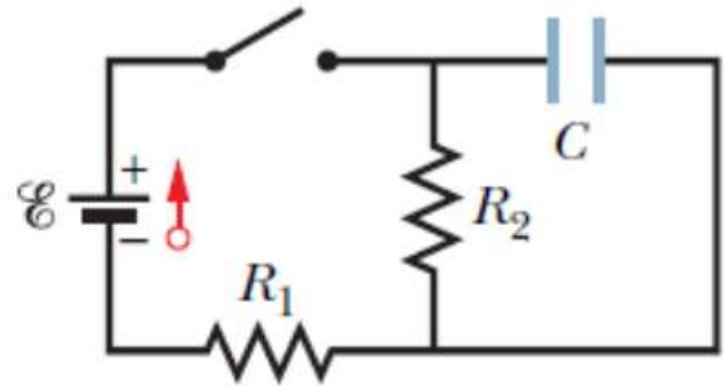Problem 13

In the figure, $R_1 = 10.0 \text{ k}\Omega$, $R_2 = 15.0 \text{ k}\Omega$, $C = 0.400 \text{ }\mu\text{F}$, and the ideal battery has emf $\epsilon = 20.0 \text{ V}$. First, the switch is closed a long time so that the steady state is reached. Then the switch is opened at time $t = 0$. What is the current in resistor 2 at $t = 4.00 \text{ ms}$? (01小題)



_____ A

29: ANS: = 4.11E-4 In the steady state situation,

$$V_0 = R_2 \frac{\epsilon}{R_1 + R_2} = (15.0 \text{ k}\Omega) \left(\frac{20.0 \text{ V}}{10.0 \text{ k}\Omega + 15.0 \text{ k}\Omega} \right) = 12.0 \text{ V}.$$

$$V = V_0 e^{-t/RC} \quad \text{after the switch is opened (at } t = 0\text{)}.$$

$$t = 0.00400 \text{ s}, \quad V = (12) e^{-0.004 / (15000)(0.4 \times 10^{-6})} = 6.16 \text{ V}.$$

the current through R_2 is $6.16 / 15000 = 4.11 \times 10^{-4} \text{ A}$.